

PHYF214 PHYSICS LAB REPORT SEM1 2018-2019  
Lab 11 Group 7: LCR Resonance and RC discharging Circuit  
[LCR]

Ashwin Kumar K - 2017A8PS1034G

25<sup>th</sup> October, 2018

## 1 Experimental Tasks

To study resonance effect in series and parallel LCR circuits.  
TO study discharge graph of RC circuit.

## 2 Apparatus

Oscillator (1 to 1 M Hz), resistors, capacitors, inductors, AC milli-ammeter, Oscilloscope.

## 3 Theory

In the series LCR circuit, an inductor (L), a capacitor (C) and a resistor (R) are connected in series with a variable frequency sinusoidal emf source and the voltage across the resistance is measured. As the frequency is varied, the current in the circuit (and hence the voltage across R) changes, becoming maximum at the resonance frequency  $\nu_0 = \frac{1}{2\pi\sqrt{LC}}$ . In the parallel LCR circuit, the current is minimum at the resonance frequency.


In and RC circuit, When a capacitor is connected to a voltage source, it charges gradually to the maximum value and the rate of charging depends upon the time constant of the circuit. Since the voltage across the capacitor is proportional to the charge stored by it, the graph of voltage v/s time can be studied to see how the capacitor discharges as a function of time.

## 4 Observations

### 4.1 LCR circuit (series and parallel)


For series LCR circuit, ( $C=0.01\mu\text{F}$ ,  $R=100\Omega$ ,  $L=10\text{mH}$ ) The expected resonance peak occurs at 15915 Hz The observation table and graph are as follows,

Frequency(Hz)	Current (in $\mu\text{A}$ )
2000	0.05
4000	0.08
6000	0.11
8000	0.15
10000	0.21
12000	0.34
14000	0.57
15000	0.75
16000	0.97
16400	1.04
16800	1.08
16900	1.08
17000	1.07
17100	1.06
17200	1.05
17600	1.03
18000	0.93
18400	0.89
18800	0.78
19000	0.74
20000	0.56
21000	0.42
22000	0.34
23000	0.25
24000	0.19
25000	0.13

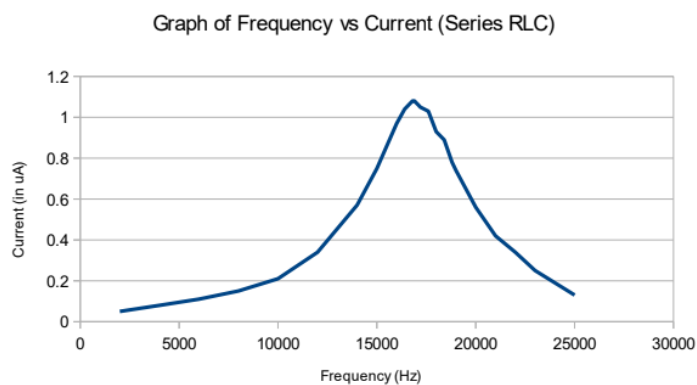


Now, for parallel LCR circuit ( $C=0.01\mu\text{F}$ ,  $R=100\Omega$ ,  $L=10\text{mH}$ ) The observation tables and graphs are shown below,

Frequency(Hz)	Current (in uA)
7	0.89
8	0.66
9	0.43
10	0.31
11	0.19
12	0.12
13	0.07
14	0.04
15	0.03
16	0.03
17	0.04
18	0.05
19	0.06
20	0.07
21	0.08
22	0.08
23	0.09
24	0.11
25	0.12
26	0.13
27	0.14
28	0.17
29	0.19

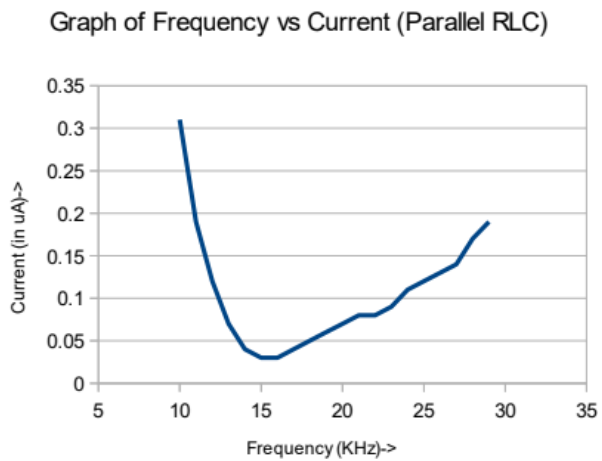
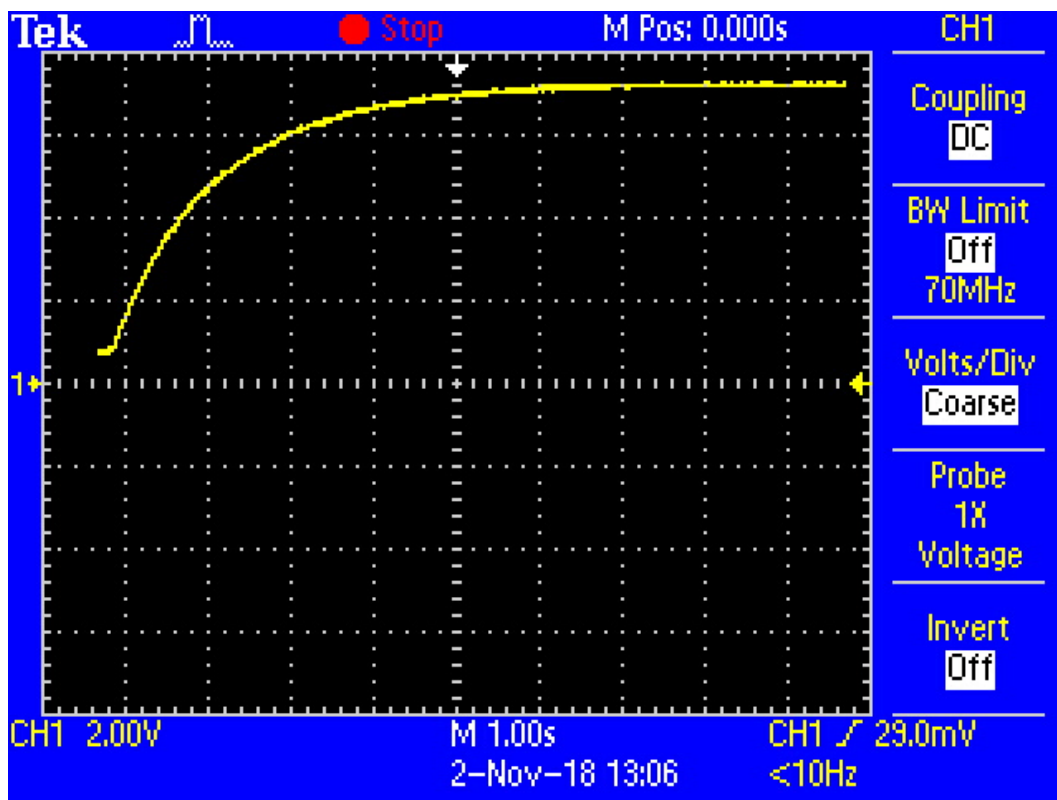
## 4.2 RC circuit

For this RC circuit source voltage was set to 8V and the capacitor was  $4.7\mu\text{F}$  the resistor was  $235\text{K}\Omega$ . The graph obtained through the Oscilloscope is as follows



## 5 *Analysis:*

### 5.1 LCR circuit

The current through Series LCR circuit is a bell shaped graph when plotted against frequency, and current through this circuit is maximum when driving frequency of source is equal to the natural frequency of the circuit. Similarly, current through the parallel LCR circuit is a well shaped graph which is well shaped and the minima occurs at natural frequency of the LCR circuit. The expected natural/resonance frequency and the obtained frequency are a little off and can be attributed to additional impedance offered by the connecting wires and errors in the values of the components used.

### 5.2 RC circuit

The Voltage across the capacitor rises to a maximum value exponentially as  $V = V_0(1 - e^{-\frac{t}{RC}})$ . The maximum obtained in the graph is a little less than the source voltage of 8V and can again be attributed to losses due to finite resistance of the connecting wires.

## 6 Precautions

- 1. Calculate the expected resonance frequency before beginning to take readings, and make sure to take sufficient number of readings in the vicinity of this frequency to be able to draw the shape of the resonance curve.
- Make sure the range of readings you take is sufficient to go beyond the half-power points on both sides of resonance.